

ENEE 381 Problem Set #4

4/1/03 due 4/10/03

- (1) Cheng problem 8-20
- (2) Cheng problem 8-21
- (3) A length of loss-less transmission line is first short-circuited at one end and then open-circuited. The impedance measured at the other end in the first case is Z_1 and Z_2 in the second. Prove that $Z_1 Z_2 = Z_0^2$. This is a convenient way for measuring the characteristic impedance of an unknown line.
- (4) A 50 ohm transmission line is terminated with an impedance of $20-j30$. What is the magnitude and phase of the reflection coefficient?
- (5) Repeat question (4) using the Smith chart
- (6) A 75 ohm transmission line is terminated with a load of $150 + j50$ ohm. Compute ρ in terms of both amplitude $|\rho|$ and ϕ . What fraction of incident power is absorbed in the load?
- (7) Cheng problem 9.26
- (8) Cheng problem 9.27
- (9) Cheng problem 9.30
- (10) Use Smith chart. A line with $Z_0 = 100\Omega$ is terminated with an unknown load. The SWR is found to be 3. A current maximum is observed 0.1λ from the load. What are:
 - (a) the load?
 - (b) the reflection coefficient ρ , magnitude and angle?
 - (c) how would you match the line without changing the load at the end of the line?
- (11) Use Smith chart. A transmission line of characteristic impedance 75 ohm is terminated with an impedance $50+j125$ ohm. 0.1λ from the load a 150ohm shorted stub 0.2λ long is connected in shunt to the main line. What are:
 - (a) The reflection coefficient in magnitude and phase at this point?
 - (b) The standing wave ratio?
 - (c) Where is the nearest current minimum that is greater than 0.1λ from the load?
 - (d) Where is the nearest point greater than 0.1λ from the load where the line can be matched with an open 75 ohm stub?
- (12) Use Smith chart. Cheng problem 9.48
- (13) Use Smith chart. Cheng problem 9-49.
- (14) Use Smith chart. Cheng problem 9-50.
- (15) Use Smith chart. Cheng problem 9-51.

SOLUTIONS

(1)

P. 8-20 a) $\delta = \frac{1}{\sqrt{\pi f \mu_0 \sigma}}$, $f = 10^4 / 2\pi$.

b) $\vec{H}(z,t) = \vec{a}_y H_0 e^{-z/\delta} \cos(10^4 t - \frac{z}{\delta})$.

$\eta_c = (1+j) \frac{\alpha}{\sigma} = (1+j) \frac{1}{\sigma \delta} = \frac{\sqrt{2}}{\sigma \delta} e^{j\pi/4}$.

$\vec{E}(z,t) = \vec{a}_x \frac{\sqrt{2}}{\sigma \delta} H_0 e^{-z/\delta} \cos(10^4 t - \frac{z}{\delta} + \frac{\pi}{4})$.

c) $\vec{P}_{av} = \frac{1}{2} \text{Re}(\vec{E} \times \vec{H}^*) = \vec{a}_z \frac{1}{2} \frac{\sqrt{2}}{\sigma \delta} H_0^2 \cos \frac{\pi}{4}$
 $= \vec{a}_z \frac{1}{2} \left(\frac{H_0^2}{\sigma \delta} \right) \quad (\text{W/m}^2)$.

(2)

P. 8-21 Given $\vec{E}_i = E_0 (\vec{a}_x - j \vec{a}_y) e^{-j\beta z}$

a) Assume reflected $\vec{E}_r(z) = (\vec{a}_x E_{rx} + \vec{a}_y E_{ry}) e^{j\beta z}$

Boundary condition at $z=0$: $\vec{E}_i(0) + \vec{E}_r(0) = 0$.

$\rightarrow \vec{E}_r(z) = E_0 (-\vec{a}_x + j \vec{a}_y) e^{j\beta z}$, a left-hand circularly polarized wave in $-z$ direction.

b) $\vec{a}_{n2} \times (\vec{H}_1 - \vec{H}_2) = \vec{J}_s \rightarrow -\vec{a}_z \times [\vec{H}_i(0) + \vec{H}_r(0)] = \vec{J}_s$. ($\vec{H}_2 = 0$ in perfect conductor)

$\vec{H}_i(0) = \frac{1}{\eta_0} \vec{a}_z \times \vec{E}_i(0) = \frac{E_0}{\eta_0} (j \vec{a}_x + \vec{a}_y)$, $\vec{H}_r(0) = \frac{1}{\eta_0} (-\vec{a}_z) \times \vec{E}_r(0) = \frac{E_0}{\eta_0} (j \vec{a}_x + \vec{a}_y)$.

$\vec{H}_1(0) = \vec{H}_i(0) + \vec{H}_r(0) = \frac{2E_0}{\eta_0} (j \vec{a}_x + \vec{a}_y)$,

$\vec{J}_s = -\vec{a}_z \times \vec{H}_1(0) = \frac{2E_0}{\eta_0} (\vec{a}_x - j \vec{a}_y)$.

c) $\vec{E}_1(z,t) = \text{Re} [\vec{E}_i(z) + \vec{E}_r(z)] e^{j\omega t}$

$= \text{Re} E_0 [(\vec{a}_x - j \vec{a}_y) e^{-j\beta z} + (-\vec{a}_x + j \vec{a}_y) e^{j\beta z}] e^{j\omega t}$

$= \text{Re} E_0 [-2j(\vec{a}_x - j \vec{a}_y) \sin \beta z] e^{j\omega t} = \text{Re} E_0 \sin \beta z (-2j \vec{a}_x + 2 \vec{a}_y) e^{j\omega t}$

$= 2 E_0 \sin \beta z (\vec{a}_x \sin \omega t - \vec{a}_y \cos \omega t)$.

(3) The impedance observed a distance l from a load Z_L on a lossless line of impedance Z_0 is

$$Z_i = Z_0 \left[\frac{Z_L \cos kl + j Z_0 \sin kl}{Z_0 \cos kl + j Z_L \sin kl} \right]$$

If the line is shorted $Z_L = 0$ and

$$Z_i = Z_1 = j Z_0 \tan kl$$

If the line is open then $Z_L \rightarrow \infty$ and

$$Z_i = Z_2 = -j Z_0 \cot kl$$

clearly $Z_1, Z_2 = Z_0^2$

(4) $Z_L = 20 - j30 \text{ ohm}$ $Z_0 = 50 \text{ ohm}$


$$\rho = \frac{20 - j30 - 50}{20 - j30 + 50} = \frac{-30 - j30}{70 - j30}$$

$$\rho = \frac{-3 - j3}{7 - j3} = \frac{-(3 + j3)(7 + j3)}{58}$$


$$\rho = \frac{-12 - j30}{58} = \frac{-6 - j15}{29}$$

$$|\rho| = 0.557$$


$$\phi = -111.8^\circ$$

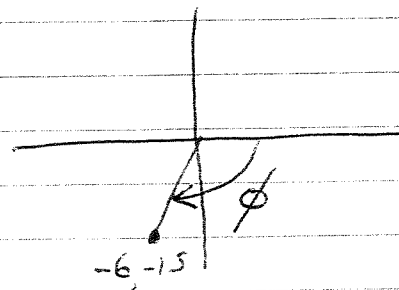

(5)

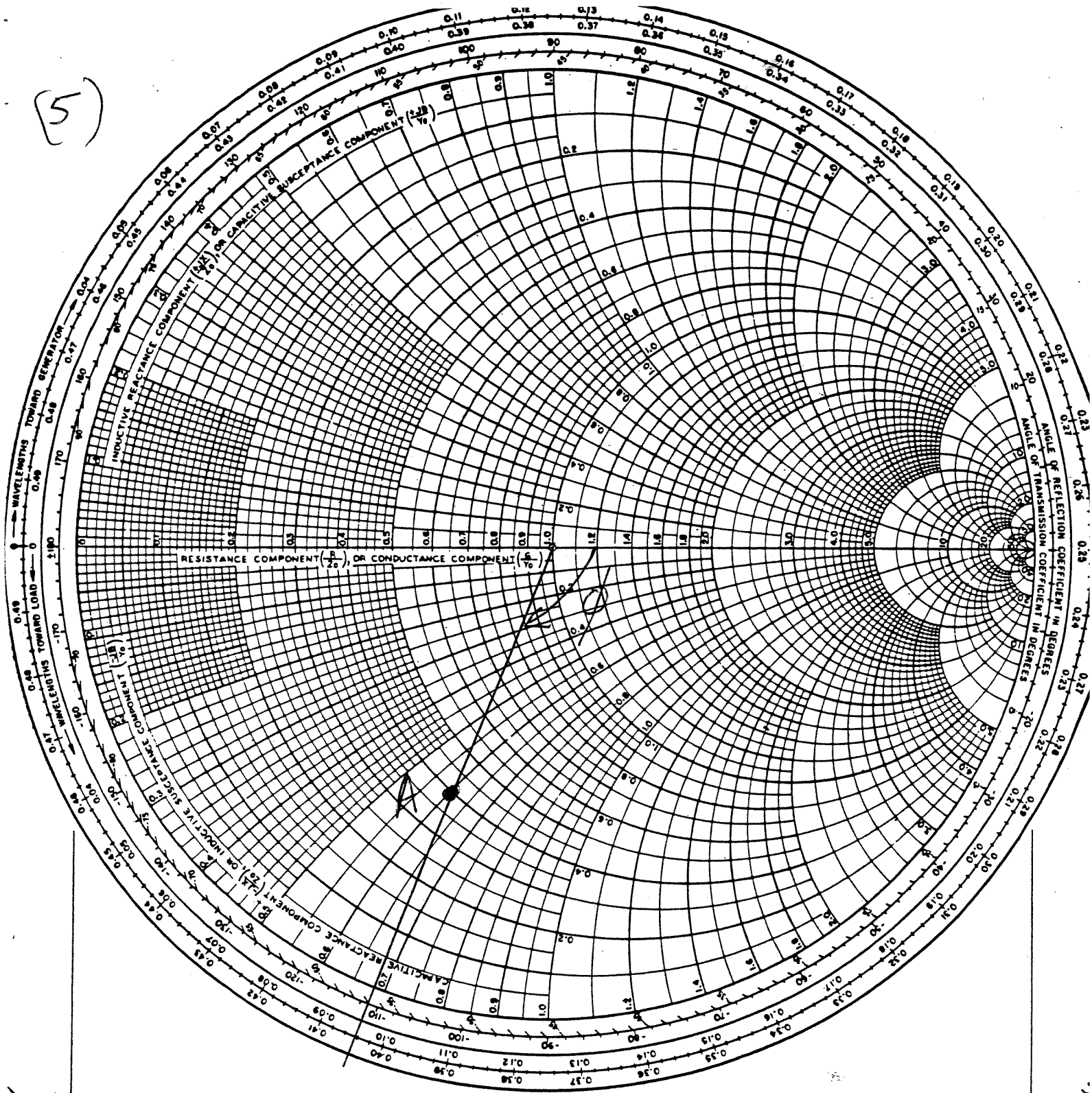

RADIALLY SCALED PARAMETERS

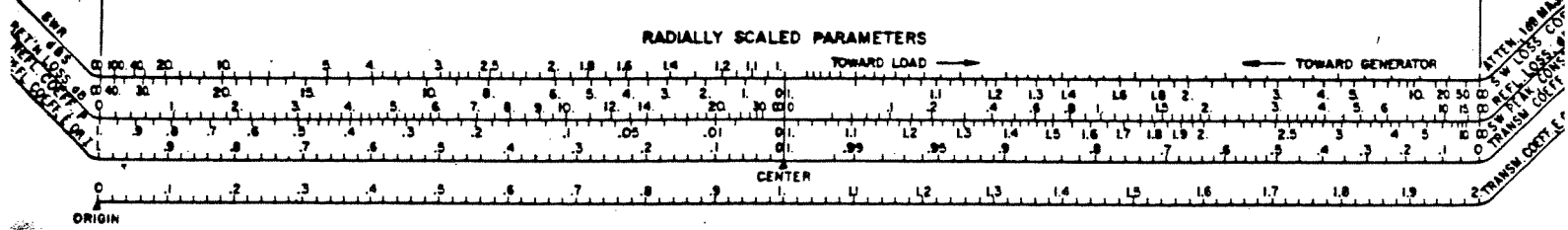

(5) see chart Normalized load is

$$Z_L = 0.4 - j0.6$$

$$|\rho| = 0.56 \quad \phi = -111.8^\circ$$

(6) $Z_L = 150 + j50$

$$Z_0 = 75$$

Normalized load $Z_L = \frac{150 + j50}{75} = 2 + j0.667$

$$\rho = \frac{Z_L - Z_0}{Z_L + Z_0} = \frac{75 + j50}{225 + j50} = \frac{3 + j2}{9 + j2} = \frac{(3 + j2)(9 - j2)}{81 + 4}$$

$$\rho = \frac{31 + 12j}{85} = |\rho| e^{j\phi}$$

$$|\rho| = \frac{1}{85} \sqrt{31^2 + 12^2} = 0.391 \quad \phi = \tan^{-1} \frac{12}{31} = 21.16^\circ$$

Fraction of energy reflected is $|\rho|^2$, Fraction into load $(1 - |\rho|^2) = 0.847$

(7) P.9-26 From Eq. (9-147): $Z_i = R'_0 \frac{Z_L + jR'_0 t}{R'_0 + jZ_L t} \rightarrow Z_L = R'_0 \frac{Z_i - jR'_0 t}{R'_0 - jZ_i t}$, $t = \tan \beta l'$

$$Z_i = R'_0 \frac{Z_L + jR'_0 t}{R'_0 + jZ_L t} \rightarrow Z_L = R'_0 \frac{Z_i - jR'_0 t}{R'_0 - jZ_i t}$$

With $Z_i = 50 \Omega$ and $Z_L = 40 + j10 \Omega$, we have

$$40 + j10 = R'_0 \frac{50 - jR'_0 t}{R'_0 - j50t} \rightarrow \begin{cases} 40R'_0 + 500t = .50R'_0 \\ 10R'_0 - 2000t = -R'_0 t \end{cases}$$

$$\therefore R'_0 = 38.7 \Omega; \quad t = \tan \beta l' = 0.775 \rightarrow l' = 0.105 \lambda$$

(8) P.9-27 a) $|\Gamma| = \frac{S-1}{S+1} = \frac{2-1}{2+1} = \frac{1}{3}$

$$\text{Eq. (9-133a): } V(z') = \frac{I_L}{2} (Z_L + Z_0) e^{j\beta z'} [1 + |\Gamma| e^{j\phi}]$$

$$\text{Eq. (9-134): } \Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma| e^{j\theta_r}, \quad \phi = \theta_r - 2\beta z'$$

Voltage is a minimum when $\phi = \pm \pi \rightarrow \theta_r = 2\left(\frac{2\pi}{\lambda}\right) \times 0.3\lambda - \pi = 0.2\pi$

$$\therefore \Gamma = \frac{1}{3} e^{j0.2\pi}$$

b) $Z_L = Z_0 \left(\frac{1 + \Gamma}{1 - \Gamma} \right) = 466 + j206 \Omega$

c) Terminating resistance $R_m = \frac{R_0}{S} = \frac{300}{2} = 150 \Omega$,

$$l_m = \frac{\lambda}{2} - z'_m = (0.5 - 0.3)\lambda = 0.2\lambda$$

Another set of solution is: $R'_m = SR_0 = 600 \Omega$ & $l'_m = 0.45\lambda$.

(9)

P. 9-30 a) Given: $V_g = 0.1 \angle 0^\circ$ (V), $Z_g = Z_o = 50$ (Ω), $R_L = 25$ (Ω)
 $= 0.5 Z_o$.

$$V_i = \frac{Z_i}{Z_o + Z_i} V_g, \quad I_i = \frac{V_g}{Z_o + Z_i},$$

$$\text{where } Z_i = Z_o \frac{0.5 Z_o + j Z_o \tan \beta l}{Z_o + j 0.5 Z_o \tan \beta l} = Z_o \frac{1 + j 2 \tan \beta l}{2 + j \tan \beta l}.$$

$$\therefore V_i = \frac{1 + j 2 \tan \beta l}{3(1 + j \tan \beta l)} V_g = \frac{1}{30} \left(\frac{1 + j 2 \tan \beta l}{1 + j \tan \beta l} \right) \text{ (V)},$$

$$I_i = \frac{2 + j \tan \beta l}{3 Z_o (1 + j \tan \beta l)} V_g = \frac{2}{3} \left(\frac{2 + j \tan \beta l}{1 + j \tan \beta l} \right) \text{ (mA)}.$$

Setting $Z_g = Z_o$ and $\Gamma_g = 0$ in Eqs. (9-120a) and (9-120b),

$$\text{we have } V_L = V(z=0) = \frac{V_g Z_o}{Z_o + Z_g} e^{-j\beta l} (1 + \Gamma) \quad \left(\Gamma = \frac{R_L - Z_o}{R_L + Z_o} = -\frac{1}{3} \right)$$

$$= \frac{1}{30} e^{-j\beta l} \text{ (V)},$$

$$I_L = I(z=0) = \frac{V_g}{Z_o + Z_g} e^{-j\beta l} (1 - \Gamma) = \frac{4}{3} e^{-j\beta l} \text{ (mA)}.$$

$$b) S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = 2.$$

$$c) (P_{av})_L = \frac{1}{2} \operatorname{Re} (V_L I_L^*) = \frac{1}{2} \left(\frac{1}{30} \right) \left(\frac{4}{3} \times 10^{-3} \right) = 2.22 \times 10^{-5} \text{ (W)}$$

$$= 0.0222 \text{ (mW)}.$$

$$\text{If } R_L = 50 \text{ } (\Omega), \quad V_L = \frac{V_g}{2} e^{-j\beta l}, \quad I_L = \frac{V_g}{2 Z_o} e^{-j\beta l}$$

$$\longrightarrow \text{Max. } (P_{av})_L = \frac{V_g^2}{8 Z_o} = 2.50 \times 10^{-5} \text{ (W)}.$$

$$(10) \quad Z_0 = 100 \Omega$$

VSWR = 3 POINT A on Chart


The current maximum is at point B
This is 0.1λ from load. Go 0.1λ towards
load from point B

point C is normalized load $0.5 - j0.6$
Actual load is $Z_L = 50 - j60$, Y_L is at point D

$$|\rho| = 0.49 \quad \phi = 252^\circ$$


Could match at $M1$ with an inductor
in parallel. $M1$ is 0.16λ towards generator

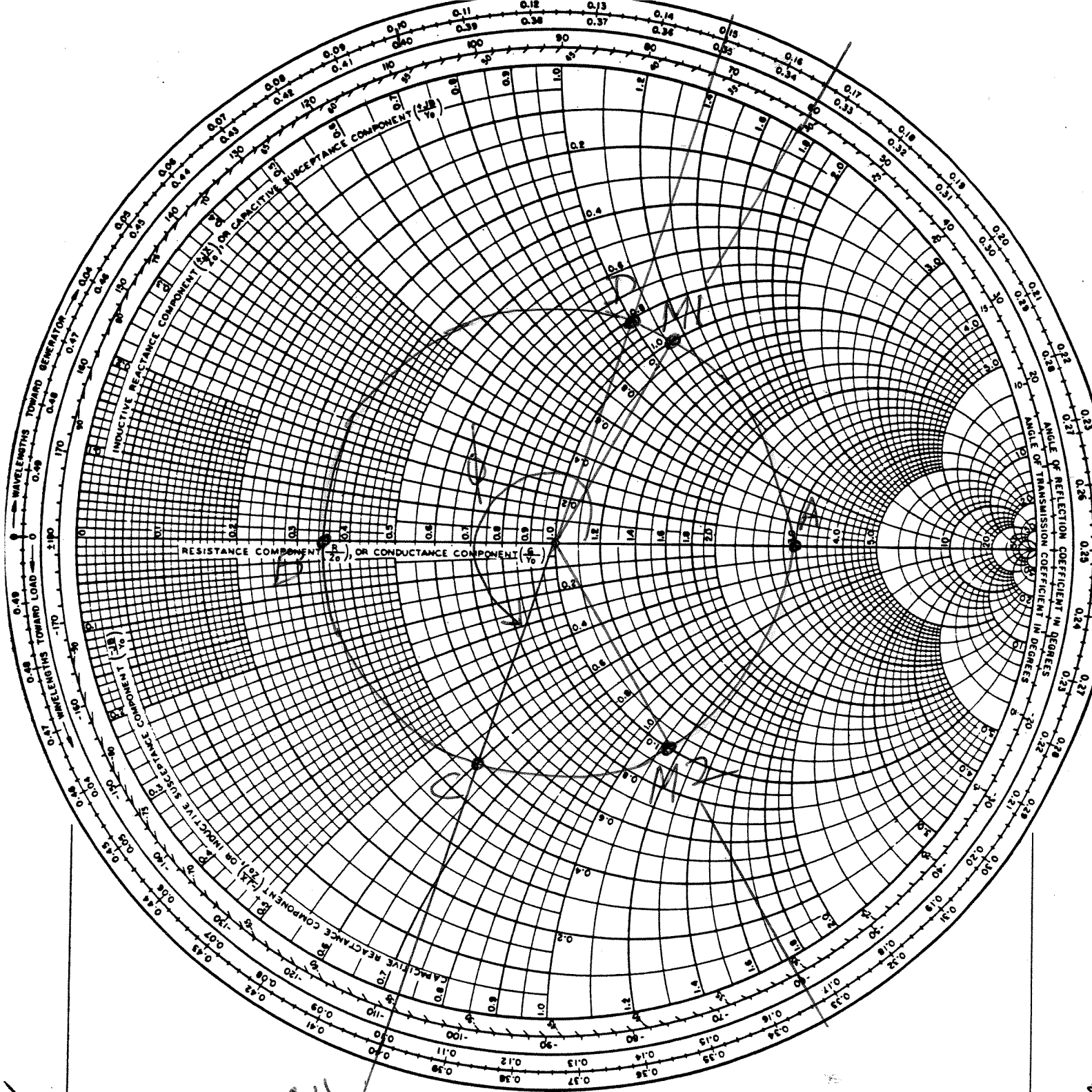Could match at $M2$ with a capacitor in
parallel. $M2$ is 0.204λ towards generator



0.1λ
TOWARDS LOAD

RADIALLY SCALED PARAMETERS

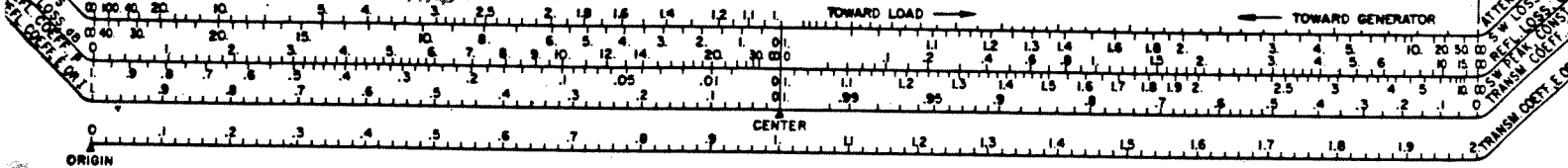

$$(11) \quad Z_L = 50 + j125 \quad Z_0 = 75$$

$$y_L = \frac{50 + j125}{75} = 0.667 + j1.667 \quad \text{POINT A}$$

y_L is normalized admittance, point B
 $y_L = 0.22 - j0.59$

0.1λ from this point, towards generator
is point C $y_C = 0.18 + j0.13$

the shorted stub 0.2λ has normalized
admittance $y_{\text{stub}} = -j0.322$

ACTUAL STUB ADMITTANCE IS $-j0.332 \times \left(\frac{1}{150}\right)$

Renormalize $y' = \frac{-j0.332 \times \left(\frac{1}{75}\right)}{(1/75)} = -j0.166$

ADD THIS TO POINT C VALUE

$$y'' = 0.18 + j0.13 - j0.166 = 0.18 - j0.036$$

POINT D


(a) $|e| = 0.7 \quad \phi = 176^\circ$

(b) $S = 5.6$

(c) Nearest current minimum to load is point E,
which is 0.081λ from load. Next current
minimum is 0.5λ further. So, ANSWER 0.581λ


(d) Nearest matching point is point M,
 $0.187 + 0.081\lambda$ FROM LOAD, 0.268λ FROM LOAD

(11)

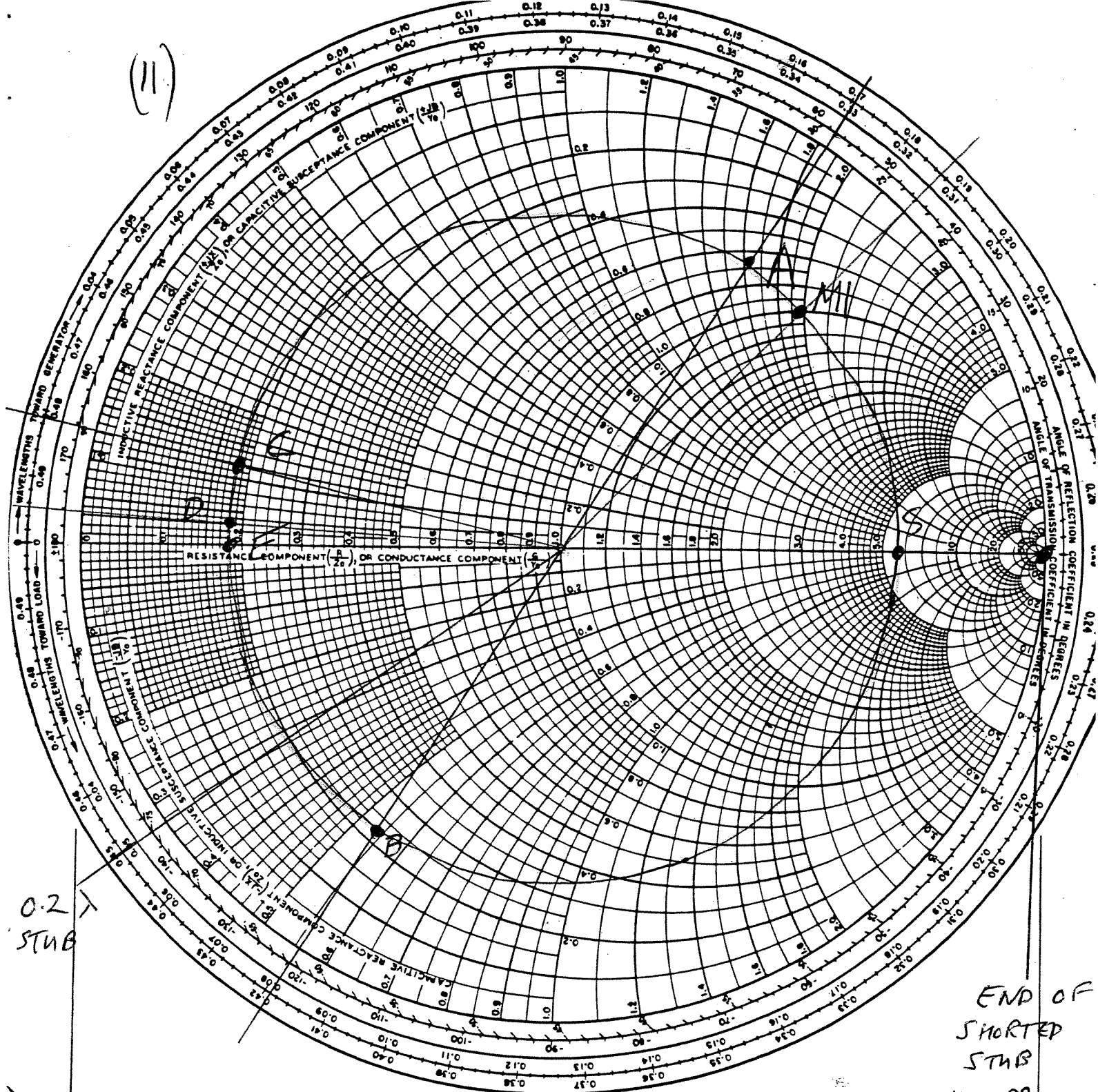

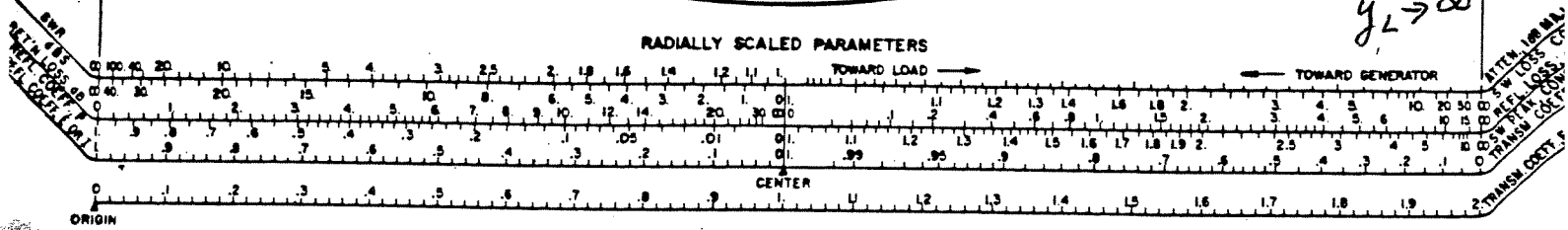
0.2 STUB

END OF SHORTED STUB $Y_L \rightarrow \infty$



(12)

P.9-48

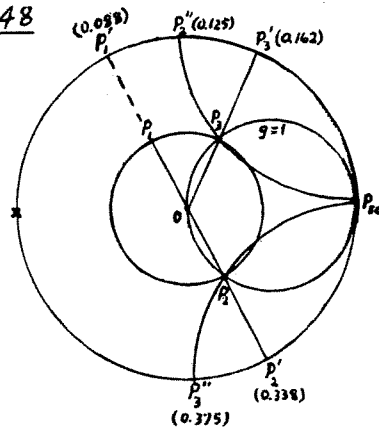

$$z_L = 0.5 + j0.5,$$

$$y_L = 1 - j.$$

a) See construction.

$$P_1: z_L = 0.5 + j0.5.$$

$$P_2: y_L = 1 - j1 = y_2 \rightarrow d_2 = 0.$$

$$P_3: y_3 = 1 + j1.$$

$$\rightarrow d_3 = 0.162\lambda + (0.5 - 0.338)\lambda = 0.324\lambda.$$

$$P_2'': b_2 = j1 \rightarrow l_2 = (0.5 + 0.125)\lambda = 0.375\lambda.$$

$$P_3'': b_3 = -j1 \rightarrow l_3 = (0.375 - 0.25)\lambda = 0.125\lambda.$$

b) For $Z_o' = 75 = 1.5 Z_o$, $Y_o' = 0.667 Y_o$.The required normalized stub admittances are $b_2' = -b_3' = \frac{j}{0.667} = j1.5$.

	$(Z_o)_{stub} = (Z_o)_{line}$	$(Z_o)_{stub} = 1.5(Z_o)_{line}$
$z_L = 0.5 + j0.5$	$d_2 = 0, l_2 = 0.375\lambda$	$d_2' = 0, l_2' = 0.406\lambda$
$y_L = 1 - j1$	$d_3 = 0.324\lambda, l_3 = 0.125\lambda$	$d_3' = 0.324\lambda, l_3' = 0.0936\lambda$

(13)

P.9-49 $z_L = 0.5 + j0.5$

Use Smith chart as an impedance chart. Same construction as that in problem P.9-34 except P_{sc} would be on the extreme left (marked by a x), and $g=1$ circle becomes $r=1$ circle.

$$P_1: z_L = 0.5 + j0.5; P_2: z_{i2} = 1 + j1 \text{ with } d_2 = (0.162 - 0.088)\lambda = 0.074\lambda.$$


$$P_3: z_{i3} = 1 - j1 \text{ with } d_3 = (0.338 - 0.088)\lambda = 0.250\lambda.$$

To achieve a match with a series stub having $R_o' = \frac{35}{50} R_o$, we need a normalized stub susceptance $-j \frac{50}{35} = -j1.43$ for solution corresponding to P_2 . From Smith chart we obtain the required stub length $l_2 = 0.347\lambda$.

Similarly for solution corresponding to P_3 , a stub with a normalized susceptance $+j1.43$ is needed, which requires a stub length $l_3 = 0.153\lambda$.

(14)

P.9-50

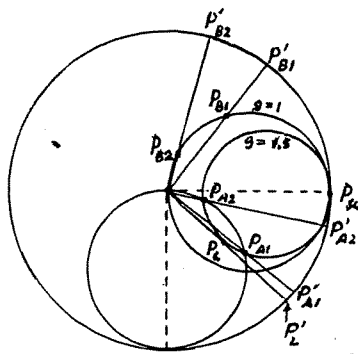

$$z_L = 0.33 + j0.33$$

$$P_L: Y_L = 1.50 - j1.50 \text{ (0.306}\lambda \text{ at } P'_L)$$

$$P_{A1}: Y_{A1} = 1.50 - j1.80 \text{ (0.304}\lambda \text{ at } P'_{A1})$$

$$P_{A2}: Y_{A2} = 1.50 - j0.14 \text{ (0.269}\lambda \text{ at } P'_{A2})$$


$$P_{B1}: Y_{B1} = 1.00 + j1.60 \text{ (0.179}\lambda \text{ at } P'_{B1})$$

$$P_{B2}: Y_{B2} = 1.00 + j0.40 \text{ (0.144}\lambda \text{ at } P'_{B2})$$

	a) Short-circuited stubs	b) Open-circuited stubs
$(Y_{SA})_1 = Y_{A1} - Y_L = -j0.30$	$l_{A1} = 0.203\lambda$	$l_{A1} = 0.453\lambda$
$(Y_{SA})_2 = Y_{A2} - Y_L = j1.36$	$l_{A2} = 0.399\lambda$	$l_{A2} = 0.149\lambda$
$(Y_{SB})_1 = -j1.60$	$l_{B1} = 0.089\lambda$	$l_{B1} = 0.339\lambda$
$(Y_{SB})_2 = -j0.40$	$l_{B2} = 0.189\lambda$	$l_{B2} = 0.439\lambda$

(15)

P.9-51

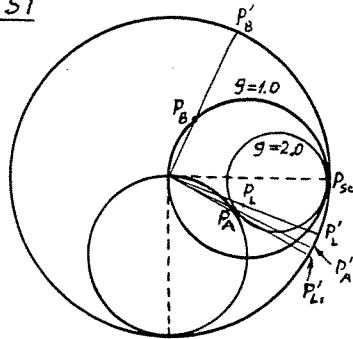

$$Y_L = \frac{300}{100 + j50} = 2.4 - j1.2$$

Point P_L on Smith chart.
(0.280 λ at P'_L)

Since the rotated $g=1.0$ circle is tangent to the $g=2.0$ circle, an added line length d_L is needed to convert g_L (2.4) to 2.0,

moving from P_L along the $|\Gamma|$ -circle to P_{L1} (not shown) on the $g=2.0$ circle (0.291 λ at P'_{L1}). Note that P_{L1} is different from P_A , the point of tangency between the $g=2.0$ and rotated $g=1.0$ circles.

a) Min. $d_L = 0.291\lambda - 0.280\lambda = 0.011\lambda$.

b) $P_A: Y_A = 2 - j1$ (0.287 λ at P'_A).

$P_B: Y_B = 1 + j1$ (0.162 λ at P'_B).

$Y_{SA} = Y_A - Y_{L1} = (2 - j1) - (2 - j1.35) = j0.35 \rightarrow l_A = 0.304\lambda$

$Y_{SB} = -j1 \rightarrow l_B = 0.125\lambda$.