

ENEE 381 Problem Set #4

4/1/04 due 4/13/04

(1) A length of loss-less transmission line is first short-circuited at one end and then open-circuited. The impedance measured at the other end in the first case is Z_1 and Z_2 in the second. Prove that $Z_1 Z_2 = Z_0^2$. This is a convenient way for measuring the characteristic impedance of an unknown line.

(2) A 50 ohm transmission line is terminated with an impedance of $20-j30$. What is the magnitude and phase of the reflection coefficient?

(3) Repeat question (4) using the Smith chart

(4) A 75 ohm transmission line is terminated with a load of $150 + j50$ ohm. Compute ρ in terms of both amplitude $|\rho|$ and ϕ . What fraction of incident power is absorbed in the load?

(5) Cheng problem 9.27

(6) Cheng problem 9.30

(7) Use Smith chart. A line with $Z_0 = 100\Omega$ is terminated with an unknown load. The SWR is found to be 3. A current maximum is observed 0.1λ from the load. What are:

(a) the load?

(b) the reflection coefficient ρ , magnitude and angle?

(c) how would you match the line without changing the load at the end of the line?

(8) Use Smith chart. A transmission line of characteristic impedance 75 ohm is terminated with an impedance $50+j125$ ohm. 0.1λ from the load a 150ohm shorted stub 0.2λ long is connected in shunt to the main line. What are:

(a) The reflection coefficient in magnitude and phase at this point?

(b) The standing wave ratio?

(c) Where is the nearest current minimum that is greater than 0.1λ from the load?

(d) Where is the nearest point greater than 0.1λ from the load where the line can be matched with an open 75 ohm stub?

(9) Use Smith chart. Cheng problem 9.48

(10) Use Smith chart. Cheng problem 9-49.

(11) Use Smith chart. Cheng problem 9-50.

(12) Use Smith chart. Cheng problem 9-51.

ENEE 381 Problem Set 4. SOLUTIONS

- (1) The transformed impedance equation is

$$Z_i = Z_0 \cdot \frac{(Z_L \cdot \cos(kl) + j \cdot Z_0 \cdot \sin(kl))}{Z_0 \cdot \cos(kl) + j \cdot Z_L \cdot \sin(kl)}$$

For a shorted line $Z_L = 0$, so

$$Z_{\text{short}} = j \cdot Z_0 \cdot \tan(kl)$$

For an open line Z_L is infinite, so

$$Z_{\text{open}} = -j \cdot Z_0 \cdot \cot(kl)$$

$$Z_{\text{short}} \cdot Z_{\text{open}} = Z_0^2 \quad \text{Q.E.D.}$$

- (2) $Z_0 := 50$ $j := i$

$$Z_L := 20 - j \cdot 30$$

$$\rho := \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\rho = -0.207 - 0.517i$$

$$|\rho| = 0.557 \quad \text{magnitude}$$

$$\frac{\arg(\rho)}{\text{deg}} = -111.801 \quad \text{phase angle in degrees}$$

- (3) On chart the normalized impedance is

$$\zeta_L := \frac{Z_L}{Z_0}$$


$$\zeta_L = 0.4 - 0.6i \quad \text{Point A on chart}$$

- (4) $Z_0 := 75$ $Z_L := 150 + j \cdot 50$


$$\rho := \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$(|\rho|)^2 = 0.153 \quad \text{Fraction of power reflected}$$

$$1 - (|\rho|)^2 = 0.847 \quad \text{Fraction of power absorbed in load}$$

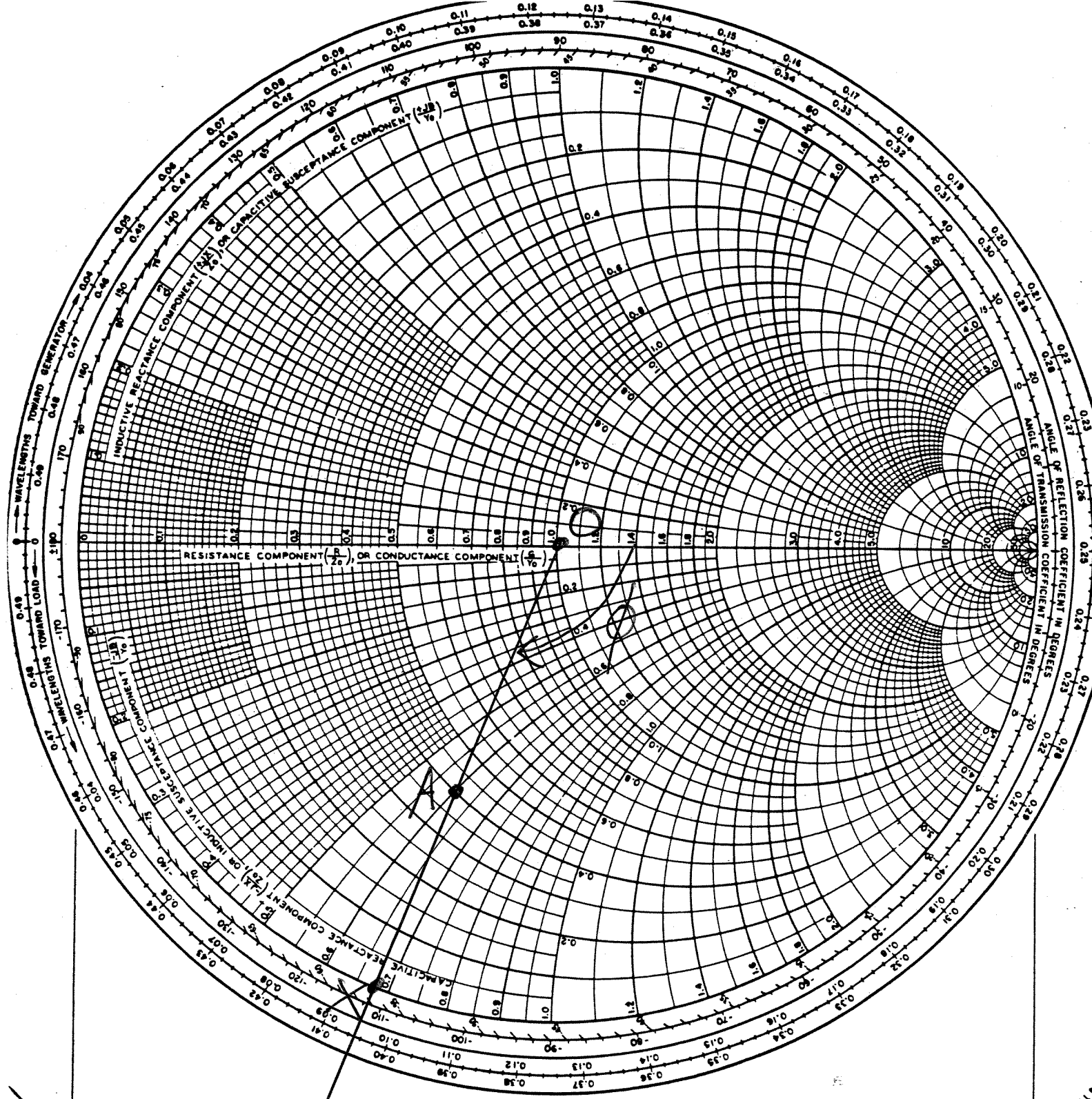

RADIALLY SCALED PARAMETERS

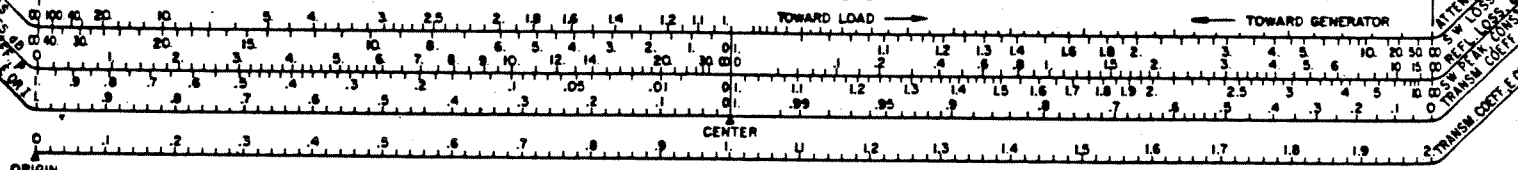

(3) $\Gamma_L = 0.4 - j0.6$

$|\Gamma| = \frac{OA}{OX} = 0.56 \quad \phi = -111^\circ$

(5) P.9-27 a) $|\Gamma| = \frac{S-1}{S+1} = \frac{2-1}{2+1} = \frac{1}{3}$.

Eq. (9-133a): $V(z') = \frac{I_0}{2}(Z_L + Z_0)e^{j\beta z'} [1 + |\Gamma|e^{j\phi}]$.

Eq. (9-134): $\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma|e^{j\theta_\Gamma}$, $\phi = \theta_\Gamma - 2\beta z'$

Voltage is a minimum when $\phi = \pm\pi \rightarrow \theta_\Gamma = 2\left(\frac{2\pi}{\lambda}\right) \times 0.3\lambda - \pi = 0.2\pi$
 $\therefore \Gamma = \frac{1}{3}e^{j0.2\pi}$

b) $Z_L = Z_0 \left(\frac{1+\Gamma}{1-\Gamma} \right) = 466 + j206 \text{ } (\Omega)$.

c) Terminating resistance $R_m = \frac{R_0}{S} = \frac{300}{2} = 150 \text{ } (\Omega)$,

$l_m = \frac{\lambda}{2} - z'_m = (0.5 - 0.3)\lambda = 0.2\lambda$.

Another set of solution is: $R'_m = SR_0 = 600 \text{ } (\Omega)$ & $l'_m = 0.45\lambda$.

(6) P.9-30 a) Given: $V_g = 0.1 \angle 0^\circ \text{ (V)}$, $Z_g = Z_0 = 50 \text{ } (\Omega)$, $R_L = 25 \text{ } (\Omega) = 0.5Z_0$.

$V_i = \frac{Z_i}{Z_0 + Z_i} V_g$, $I_i = \frac{V_g}{Z_0 + Z_i}$,

where $Z_i = Z_0 \frac{0.5Z_0 + jZ_0 \tan \beta l}{Z_0 + j0.5Z_0 \tan \beta l} = Z_0 \frac{1 + j2 \tan \beta l}{2 + j \tan \beta l}$.

$\therefore V_i = \frac{1 + j2 \tan \beta l}{3(1 + j \tan \beta l)} V_g = \frac{1}{30} \left(\frac{1 + j2 \tan \beta l}{1 + j \tan \beta l} \right) \text{ (V)}$,

$I_i = \frac{2 + j \tan \beta l}{3Z_0(1 + j \tan \beta l)} V_g = \frac{2}{3} \left(\frac{2 + j \tan \beta l}{1 + j \tan \beta l} \right) \text{ (mA)}$.

Setting $Z_g = Z_0$ and $\Gamma_g = 0$ in Eqs. (9-120a) and (9-120b),

we have $V_L = V(z'=0) = \frac{V_g Z_0}{Z_0 + Z_g} e^{-j\beta l} (1 + \Gamma)$ ($\Gamma = \frac{R_L - Z_0}{R_L + Z_0} = -\frac{1}{3}$)
 $= \frac{1}{30} e^{-j\beta l} \text{ (V)}$,

$I_L = I(z'=0) = \frac{V_g}{Z_0 + Z_g} e^{-j\beta l} (1 - \Gamma) = \frac{4}{3} e^{-j\beta l} \text{ (mA)}$.

b) $S = \frac{1+|\Gamma|}{1-|\Gamma|} = 2$.

c) $(P_{av})_L = \frac{1}{2} \text{Re}(V_L I_L^*) = \frac{1}{2} \left(\frac{1}{30} \right) \left(\frac{4}{3} \times 10^{-3} \right) = 2.22 \times 10^{-5} \text{ (W)}$
 $= 0.0222 \text{ (mW)}$.

If $R_L = 50 \text{ } (\Omega)$, $V_L = \frac{V_g}{2} e^{-j\beta l}$, $I_L = \frac{V_g}{2Z_0} e^{-j\beta l}$

$\rightarrow \text{Max. } (P_{av})_L = \frac{V_g^2}{8Z_0} = 2.50 \times 10^{-5} \text{ (W)}$.

$$(7) \quad Z_0 := 100 \quad S := 3$$

On chart mark point on real axis for $S=3$, draw circle about center of chart I_{\max} is on left hand side. Load is 0.1λ away at point $0.5-j0.6$

$$|\rho| = 0.49 \quad \phi = 108 \text{ degrees}$$

Sanity check

$$\zeta_L := 0.5 - j \cdot 0.6$$

$$Z_L := Z_0 \cdot \zeta_L$$

$$\rho := \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$|\rho| = 0.483 \quad \frac{\arg(\rho)}{\text{deg}} = -108.004$$

Matching points are at B or C. You can match with series or parallel components but the distances from the load vary depending on whether you use the chart in impedance or admittance

$$(8) \quad Z_0 := 75 \quad Z_L := 50 + j \cdot 125$$

$$\zeta_L := \frac{Z_L}{Z_0} \quad \text{Normalized load}$$

$$\zeta_L = 0.667 + 1.667i \quad \text{point A}$$

$$y_L := \frac{1}{\zeta_L}$$

$$y_L = 0.207 - 0.517i \quad \text{Normalized admittance of load, point B}$$

Shorted stub 0.2λ long starts at point C and has its normalized admittance at point D

$$y_{\text{stub150}} := -j \cdot 0.32$$

$$\text{Renormalized} \quad Y_{\text{stub}} := \frac{1}{150} \cdot y_{\text{stub150}} \quad \text{multiplying by admittance of 150 ohm line}$$

Normalize again but this time to 75 ohm line

$$y_{\text{stub75}} := \frac{Y_{\text{stub}}}{\frac{1}{75}}$$

$$y_{\text{stub75}} = -0.16i$$

0.1λ from the load is point E, where

$$y_i := 0.17 + j \cdot 0.14$$

After adding stub


$$y_{\text{total}} := y_i + y_{\text{stub75}}$$

$$y_{\text{total}} = 0.17 - 0.02i \quad \text{Point F}$$

See chart for rest of problem

(9)

P.9-48

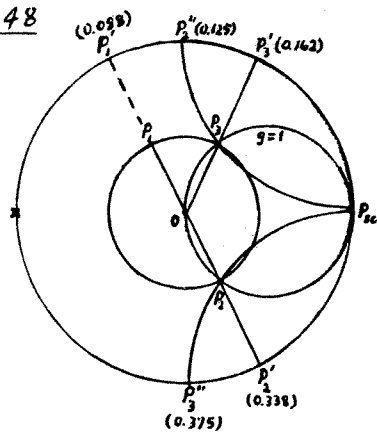

$z_L = 0.5 + j0.5$
 $y_L = 1 - j$

a) See construction.

$P_1: z_L = 0.5 + j0.5$
 $P_2: y_L = 1 - j = y_2 \rightarrow d_2 = 0$
 $P_3: y_3 = 1 + j$
 $\rightarrow d_3 = 0.162\lambda + (0.5 - 0.318)\lambda = 0.324\lambda$
 $P_2' : b_2 = j1 \rightarrow l_2 = (0.5 + 0.125)\lambda = 0.375\lambda$
 $P_3' : b_3 = -j1 \rightarrow l_3 = (0.375 - 0.25)\lambda = 0.125\lambda$

b) For $Z'_0 = 75 = 1.5 Z_0$, $Y'_0 = 0.667 Y_0$.

The required normalized stub admittances are $b'_2 = -b'_3 = \frac{j}{0.667} = j1.5$.

	$(Z_0)_{stub} = (Z_0)_{line}$	$(Z_0)_{stub} = 1.5(Z_0)_{line}$
$z_L = 0.5 + j0.5$	$d_2 = 0, l_2 = 0.375\lambda$	$d'_2 = 0, l'_2 = 0.406\lambda$
$y_L = 1 - j1$	$d_3 = 0.324\lambda, l_3 = 0.125\lambda$	$d'_3 = 0.324\lambda, l'_3 = 0.0936\lambda$

(10)

P.9-49 $z_L = 0.5 + j0.5$

Use Smith chart as an impedance chart. Same construction as that in problem P.9-34 except P_{sc} would be on the extreme left (marked by a *), and $g=1$ circle becomes $r=1$ circle.

$P_1: z_L = 0.5 + j0.5; P_2: z_{i2} = 1 + j1$ with $d_2 = (0.162 - 0.088)\lambda = 0.074\lambda$.


$P_3: z_{i3} = 1 - j1$ with $d_3 = (0.338 - 0.088)\lambda = 0.250\lambda$.

To achieve a match with a series stub having $R'_0 = \frac{35}{50} R_0$, we need a normalized stub susceptance $-j \frac{50}{35} = -j1.43$ for solution corresponding to P_2 . From Smith chart we obtain the required stub length $l_2 = 0.347\lambda$.

Similarly for solution corresponding to P_3 , a stub with a normalized susceptance $+j1.43$ is needed, which requires a stub length $l_3 = 0.153\lambda$.

(11)

P.9-50

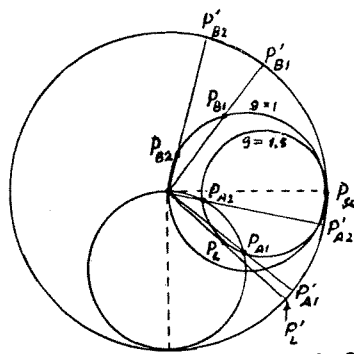

$$z_L = 0.33 + j0.33$$

$$P_L: Y_L = 1.50 - j1.50 \text{ (0.306}\lambda \text{ at } P'_L)$$

$$P_{A1}: Y_{A1} = 1.50 - j1.80 \text{ (0.304}\lambda \text{ at } P'_{A1})$$

$$P_{A2}: Y_{A2} = 1.50 - j0.14 \text{ (0.269}\lambda \text{ at } P'_{A2})$$

$$P_{B1}: Y_{B1} = 1.00 + j1.60 \text{ (0.179}\lambda \text{ at } P'_{B1})$$


$$P_{B2}: Y_{B2} = 1.00 + j0.40 \text{ (0.144}\lambda \text{ at } P'_{B2})$$

a) Short-circuited stubs b) Open-circuited stubs

$(Y_{SA})_1 = Y_{A1} - Y_L = -j0.30$	$l_{A1} = 0.203\lambda$	$l_{A1} = 0.453\lambda$
$(Y_{SA})_2 = Y_{A2} - Y_L = j1.36$	$l_{A2} = 0.399\lambda$	$l_{A2} = 0.149\lambda$
$(Y_{SB})_1 = -j1.60$	$l_{B1} = 0.089\lambda$	$l_{B1} = 0.339\lambda$
$(Y_{SB})_2 = -j0.40$	$l_{B2} = 0.189\lambda$	$l_{B2} = 0.439\lambda$

(12)

P.9-51

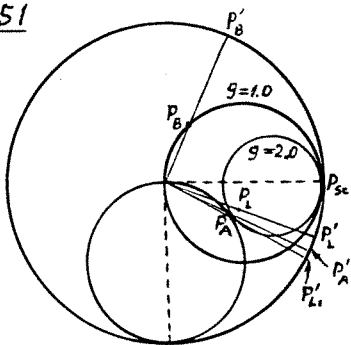

$$Y_L = \frac{100}{100 + j50} = 2.4 - j1.2$$

Point P_L on Smith chart.
(0.280 λ at P'_L)

Since the rotated $g=1.0$ circle is tangent to the $g=2.0$ circle, an added line length d_L is needed to convert g_L (2.4) to 2.0, moving from P_L along the $|\Gamma|$ -circle to P_{L1} (not shown) on the $g=2.0$ circle (0.291 λ at P'_{L1}). Note that P_{L1} is different from P_A , the point of tangency between the $g=2.0$ and rotated $g=1.0$ circles.

a) Min. $d_L = 0.291\lambda - 0.280\lambda = 0.011\lambda$.

b) $P_A: Y_A = 2 - j1$ (0.287 λ at P'_A).

$P_B: Y_B = 1 + j1$ (0.162 λ at P'_B).

$$Y_{SA} = Y_A - Y_{L1} = (2 - j1) - (2 - j1.35) = j0.35 \rightarrow l_A = 0.304\lambda$$

$$Y_{SB} = -j1 \rightarrow l_B = 0.125\lambda$$